Outline

Project Description
Roles and Responsibilities
Design Flow
System-level Design
Problem Statement
Proposed Solution
Behavioral Modeling
Comparator
Digital-to-Analog Converter
Successive Approximation
Register
Transistor-level Design

Comparator
Digital-to-Analog Converter
Layout
Comparator
Digital-to-Analog Converter
Simulations
Sinusoidal Stimulus
Ramp Stimulus
Spectrum
Figures of Merit
Conclusions
References