

IL2239 - Course Project

Design of a SAR ADC

J. Altayó B. Sunedahl

March of 2019

Outline

Project Description

Roles and Responsibilities

Design Flow

System-level Design

- Problem Statement

- Proposed Solution

- Behavioral Modeling

 - Comparator

 - Digital-to-Analog Converter

 - Successive Approximation

 - Register

Transistor-level Design

Comparator

Digital-to-Analog Converter

Layout

Comparator

Digital-to-Analog Converter

Simulations

Sinusoidal Stimulus

Ramp Stimulus

Spectrum

Figures of Merit

Conclusions

References

Project Description

Design of a single-ended SAR ADC with the following specifications.

- ▶ Comparator clock frequency: 100 MHz
- ▶ SNDR > 28 dB and SFDR > 37 dB
- ▶ Technology: 150 nm CMOS
- ▶ Supply voltage: 1.8 V
- ▶ Input amplitude (V_{in}): $0.5 V_{pp}$
- ▶ Input common-mode voltage: $0 \leq V_{in,cm} \leq 1.8$ V
- ▶ Voltage reference: $V_{ref} \leq 1.8$ V
- ▶ Switching energy below 30 pJ for $V_{in} = 300$ mV

Roles and Responsibilities

Jordi:

- ▶ Comparator
- ▶ Successive Approximation Register
- ▶ Comparator Layout

Björn:

- ▶ Digital-to-Analog Converter
- ▶ Sample & Hold
- ▶ DAC Layout

Design Flow

We used a top-down design approach:

1. System-level design
2. Behavioral modeling using Verilog-AMS
3. Transistor level modeling
4. Layout

Design Flow

We used a top-down design approach:

1. System-level design
2. Behavioral modeling using Verilog-AMS
3. Transistor level modeling
4. Layout

Co-simulations where also used to test individual blocks functionality

Outline

Project Description

Roles and Responsibilities

Design Flow

System-level Design

- Problem Statement

- Proposed Solution

- Behavioral Modeling

 - Comparator

 - Digital-to-Analog Converter

 - Successive Approximation

 - Register

Transistor-level Design

Comparator

Digital-to-Analog Converter

Layout

Comparator

Digital-to-Analog Converter

Simulations

Sinusoidal Stimulus

Ramp Stimulus

Spectrum

Figures of Merit


Conclusions

References

System-level Design I

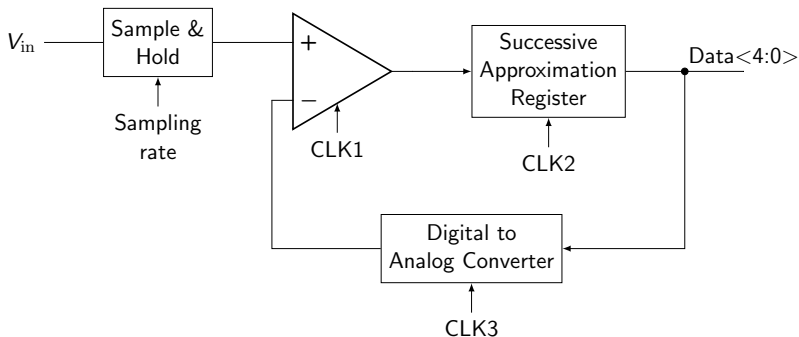Problem Statement

The basic block diagram of a SAR ADC looks as follows



System-level Design II

Proposed Solution

The following topology was used:

- ▶ Comparator: **Strong ARM Latch**
 - Reduced power consumption
 - Fast operation
 - Small area

System-level Design II

Proposed Solution

The following topology was used:

- ▶ Comparator: **Strong ARM Latch**
 - Reduced power consumption
 - Fast operation
 - Small area
- ▶ DAC: **Charge redistribution weighted capacitors**
 - Suitable for CMOS technology
 - Integrates the Sample & Hold

System-level Design II

Proposed Solution

The following topology was used:

- ▶ Comparator: **Strong ARM Latch**
 - Reduced power consumption
 - Fast operation
 - Small area
- ▶ DAC: **Charge redistribution weighted capacitors**
 - Suitable for CMOS technology
 - Integrates the Sample & Hold
- ▶ SAR: **Successive Approximation Register**
 - Integrates controls for Sample & Hold
 - Implemented as 7 state FSM
 - Verilog model

System-level Design III

Behavioral Modeling I

Comparator modeling:

```
1  always @(posedge CLK) begin
2      #5
3      outn = 0; outp = 0;
4  end
5  always @(negedge CLK) begin
6      if(V(inp) > V(inn)) begin
7          #50
8          outp = 1; outn = 0;
9      end else begin
10         #50
11         outp = 0; outn = 1;
12     end
13 end
```

Some delay was added to the behavioral model.

System-level Design III

Behavioral Modeling II


Digital-to-Analog Converter modeling:

```
1 analog begin
2     always @(posedge CLK) begin
3         for(i=0, i < 5, i++) begin
4             result += input[5-i] * Vref/(1<<i);
5         end
6         V(out) <+ transition(result, 1ns, 0.1ns, 0.1ns)
7     end
8 end
```

System-level Design III

Behavioral Modeling III

SAR algorithm: binary search

 


Assume $V_{in} = 0.7V$, $V_{ref} = 1V$
and 4 bits

System-level Design III

Behavioral Modeling III

SAR algorithm: binary search

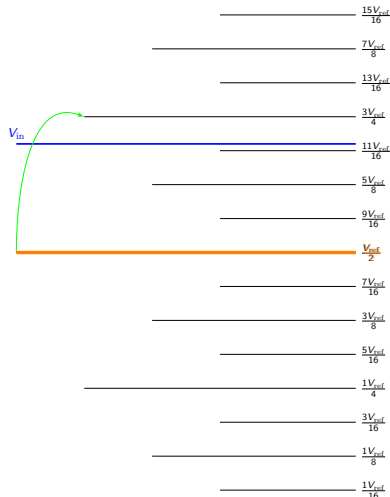


Assume $V_{in} = 0.7V$, $V_{ref} = 1V$
and 4 bits

1. $V_{in} \stackrel{?}{\geq} \frac{V_{ref}}{2}$ ✓

System-level Design III

Behavioral Modeling III

SAR algorithm: binary search

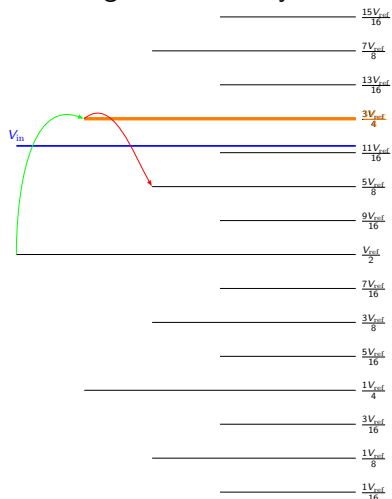

Assume $V_{in} = 0.7V$, $V_{ref} = 1V$
and 4 bits


1. $V_{in} \stackrel{?}{\geq} \frac{V_{ref}}{2}$ ✓

2. $V_{in} \stackrel{?}{\geq} \frac{3V_{ref}}{4}$ ✗

System-level Design III

Behavioral Modeling III

SAR algorithm: binary search

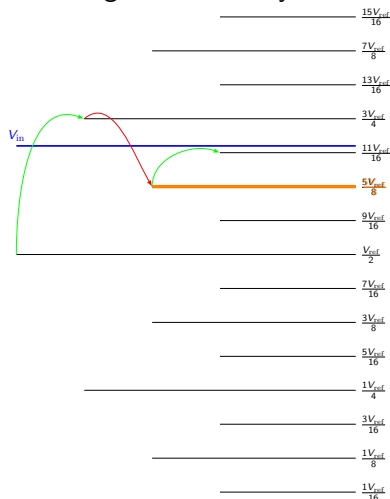


Assume $V_{in} = 0.7V$, $V_{ref} = 1V$
and 4 bits

1. $V_{in} \stackrel{?}{\geq} \frac{V_{ref}}{2}$ ✓
2. $V_{in} \stackrel{?}{\geq} \frac{3V_{ref}}{4}$ ✗
3. $V_{in} \stackrel{?}{\geq} \frac{5V_{ref}}{8}$ ✓

System-level Design III

Behavioral Modeling III

SAR algorithm: binary search

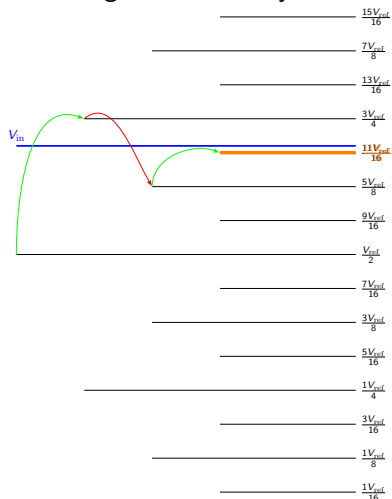


Assume $V_{in} = 0.7V$, $V_{ref} = 1V$
and 4 bits

1. $V_{in} \geq \frac{V_{ref}}{2}$ ✓
2. $V_{in} \geq \frac{3V_{ref}}{4}$ ✗
3. $V_{in} \geq \frac{5V_{ref}}{8}$ ✓
4. $V_{in} \geq \frac{11V_{ref}}{16}$ ✓

System-level Design III

Behavioral Modeling III

SAR algorithm: binary search

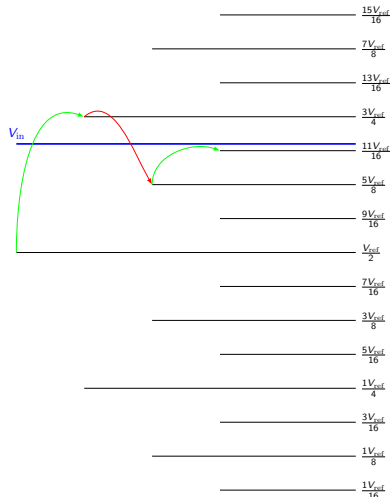

Assume $V_{in} = 0.7V$, $V_{ref} = 1V$
and 4 bits

1. $V_{in} \geq \frac{V_{ref}}{2}$ ✓
2. $V_{in} \geq \frac{3V_{ref}}{4}$ ✗
3. $V_{in} \geq \frac{5V_{ref}}{8}$ ✓
4. $V_{in} \geq \frac{11V_{ref}}{16}$ ✓

Out = 0b1011 ($\frac{11V_{ref}}{16}$)

Outline

Project Description

Roles and Responsibilities

Design Flow

System-level Design

- Problem Statement

- Proposed Solution

- Behavioral Modeling

 - Comparator

 - Digital-to-Analog Converter

 - Successive Approximation

 - Register

Transistor-level Design

Comparator

Digital-to-Analog Converter

Layout

Comparator

Digital-to-Analog Converter

Simulations

Sinusoidal Stimulus

Ramp Stimulus

Spectrum

Figures of Merit


Conclusions

References

Transistor-level Design I

Comparator


Strong ARM Latch topology

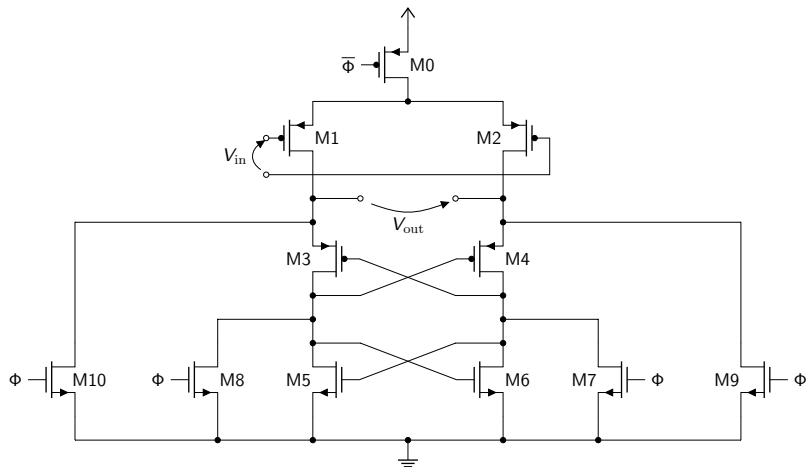

Transistor-level Design II

Digital-to-Analog Converter I


Example with 3 bit

 

Transistor-level Design II

Digital-to-Analog Converter II

Sample phase:

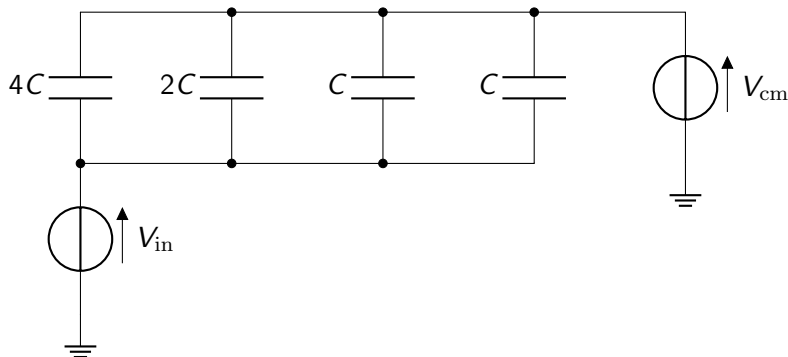


Transistor-level Design II

Digital-to-Analog Converter II

Cycling phase:

Input word: 0b100

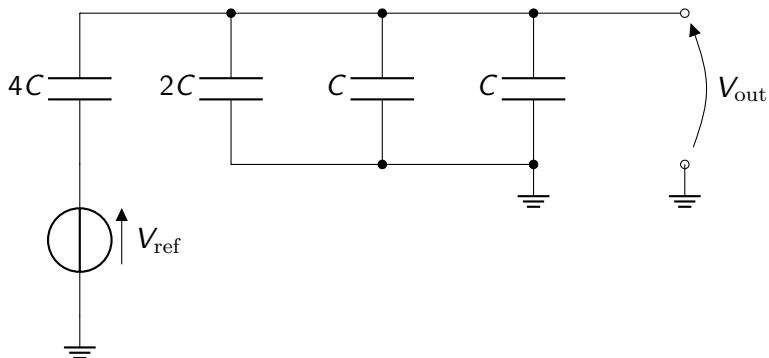


Transistor-level Design II

Digital-to-Analog Converter II

Equivalent circuit:

Input word: 0b100

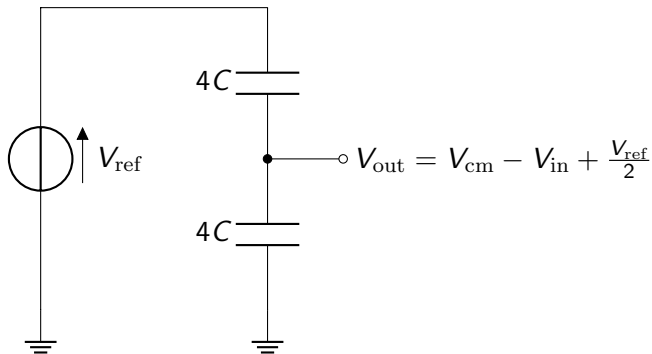


Transistor-level Design II

Digital-to-Analog Converter II

Cycling phase:

Input word: 0b010

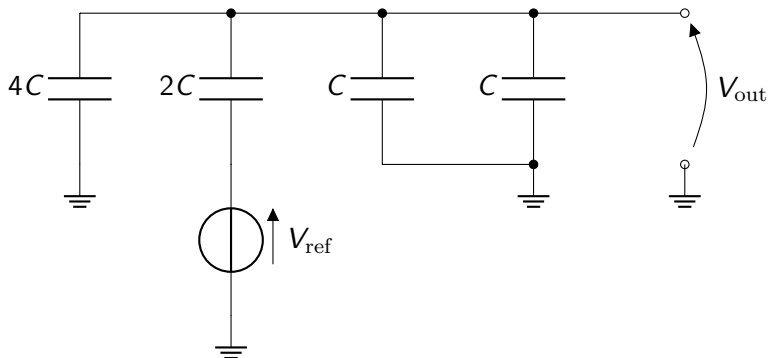


Transistor-level Design II

Digital-to-Analog Converter II

Equivalent circuit:

Input word: 0b010

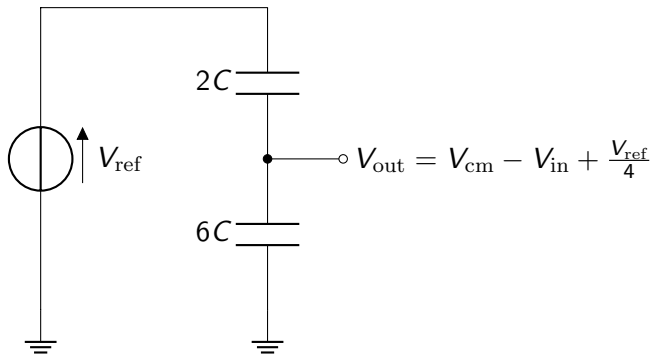

Outline

Project Description

Roles and Responsibilities

Design Flow

System-level Design

- Problem Statement

- Proposed Solution

- Behavioral Modeling

 - Comparator

 - Digital-to-Analog Converter

 - Successive Approximation

 - Register

Transistor-level Design

Comparator

Digital-to-Analog Converter

Layout

Comparator

Digital-to-Analog Converter

Simulations

Sinusoidal Stimulus

Ramp Stimulus

Spectrum


Figures of Merit

Conclusions

References

Layout I


Comparator

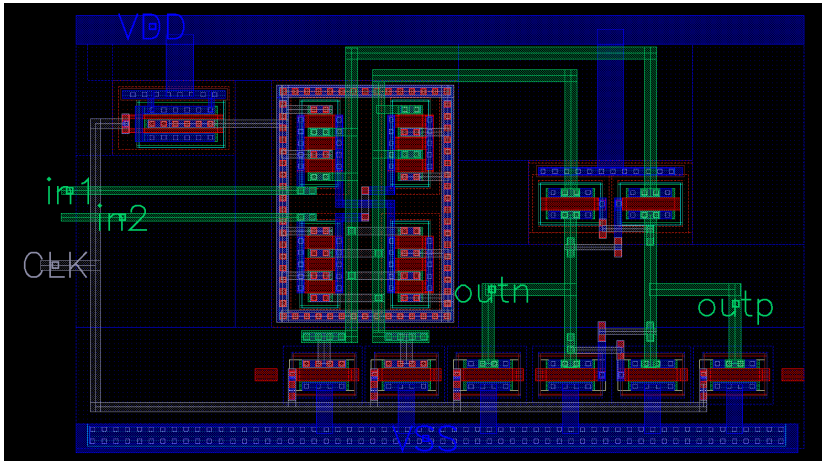

- ▶ Common centroid for the differential input pair

Layout I

Comparator

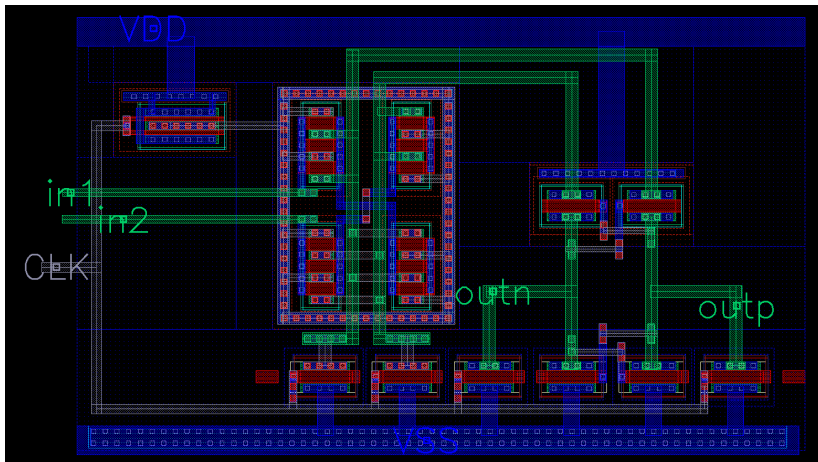


- ▶ Common centroid for the differential input pair
- ▶ Guard ring around sensitive high impedance nodes

Layout II

Digital-to-Analog Converter I

To ensure good matching we used:

- ▶ Common centroid technique

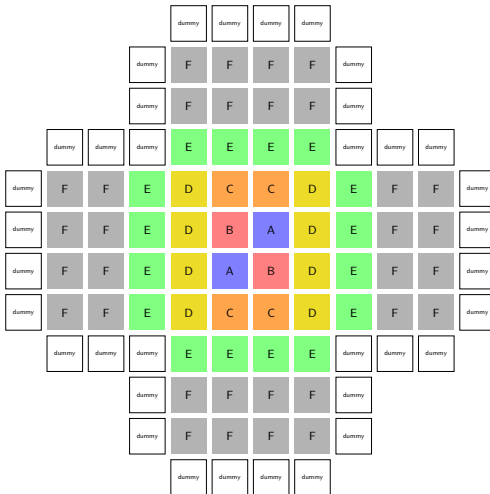


Layout II

Digital-to-Analog Converter I

To ensure good matching we used:

- ▶ Common centroid technique
- ▶ Base unit of half the minimum capacitance

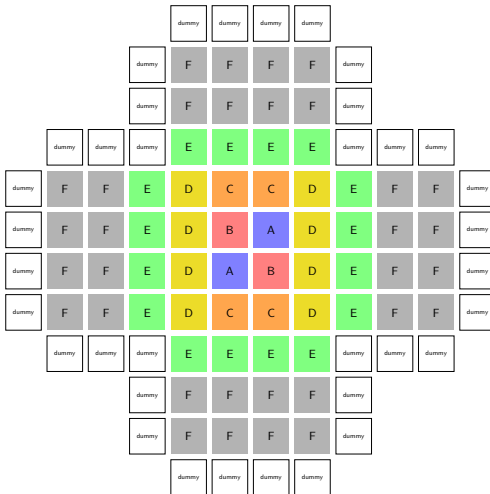


Layout II

Digital-to-Analog Converter I


To ensure good matching we used:

- ▶ Common centroid technique
- ▶ Base unit of half the minimum capacitance
- ▶ Dummy capacitors at the edges

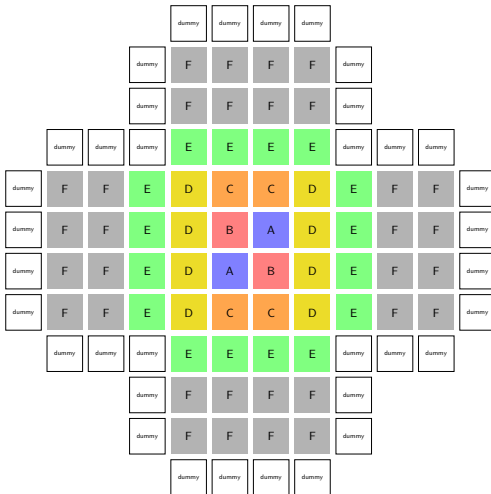

Layout II

Digital-to-Analog Converter II

 

Outline

Project Description

Roles and Responsibilities

Design Flow

System-level Design

- Problem Statement

- Proposed Solution

- Behavioral Modeling

 - Comparator

 - Digital-to-Analog Converter

 - Successive Approximation

 - Register

Transistor-level Design

Comparator

Digital-to-Analog Converter

Layout

Comparator

Digital-to-Analog Converter

Simulations

- Sinusoidal Stimulus

- Ramp Stimulus

- Spectrum



Figures of Merit

Conclusions

References



Simulations I

Sinusoidal Stimulus

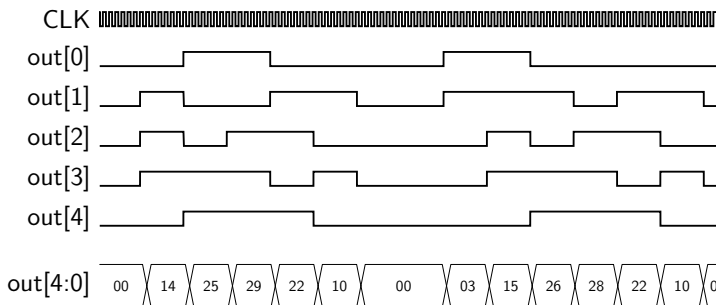 


Simulations II

Ramp Stimulus

  

Simulations III

Spectrum

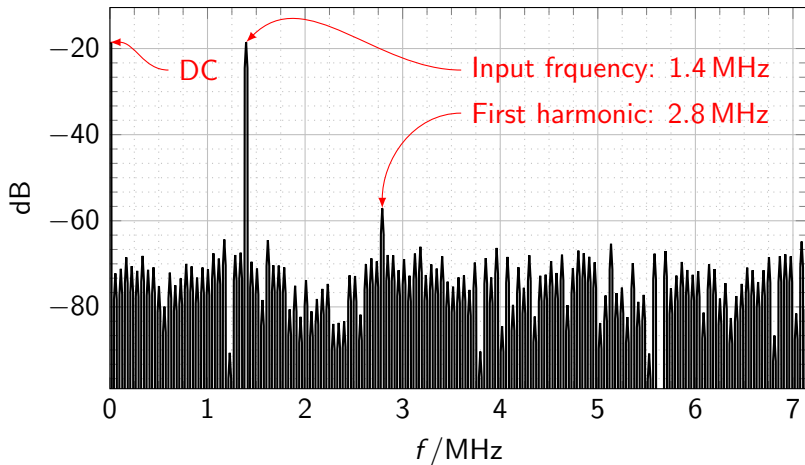

$$V_{\text{in}}, V_{\text{cm}} = 250 \text{ mV} \rightarrow -12.7 \text{ dB}$$

Figures of Merit

Sample rate	14.29 MHz
Resolution	5 bits
Full scale	500 mV
V_{ref}	500 mV
V_{cm}	250 mV
V_{LSB}	15.63 mV
ENOB	4.78
SNDR	30.55 dB
SFDR	38.16 dB
THD	1.44 %
INL	10.22 mV
DNL	8.32 mV
Energy per cycle	4.02 pJ

Conclusions

We were able to:

- ▶ Work on a state-of-the-art ADC topology

Conclusions

We were able to:

- ▶ Work on a state-of-the-art ADC topology
- ▶ Learn behavioral modeling techniques

Conclusions

We were able to:

- ▶ Work on a state-of-the-art ADC topology
- ▶ Learn behavioral modeling techniques
- ▶ Hands-on experience with charge redistribution circuits

Conclusions

We were able to:

- ▶ Work on a state-of-the-art ADC topology
- ▶ Learn behavioral modeling techniques
- ▶ Hands-on experience with charge redistribution circuits
- ▶ Gained knowledge about mixed-signal design and simulations

References

-  A. Rusu, *IL2238 & IL2239 Lecture Slides*, KTH 2018.
-  N. Ivanisevic, P. Chaourani, M. Waqar and D. I. Albertsson, *Course Tutorials*, KTH 2018.
-  T.C. Carusone, D. Johns and K. Martin, *Analog Integrated Circuit Design*, Wiley 2011.
-  C. Saint and J. Saing, *IC Mask Design: Essential Layout Techniques*, McGraw-Hill Professional Engineering 2002.
-  B. Razavi, *Principles of Data Conversion System Design*, Wiley 1995.